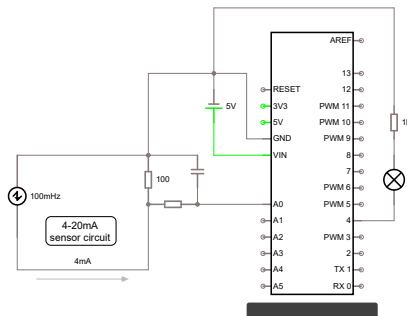




iCircuit

Arduino 4-20mA sensor

By **step**



Sample of connecting a 4-20mA sensor to an Arduino through a simple shunt resistor. Also includes a capacitor for low pass filtering of noisy input signals.

```
void setup()
{
  Serial.begin(9600);
  pinMode(A0, INPUT);
  pinMode(4, OUTPUT);
  digitalWrite(4, HIGH);
}

void loop()
{
  int r = analogRead(A0);
  Serial.print("A0: ");
  Serial.println(r);

  if( r > 200 ) {
    digitalWrite(4, HIGH);
  } else {
    digitalWrite(4, LOW);
  }
}
```

Download
Circuit

Download SVG File

elements **8**
 posted **4 years ago**
 updated **4 years ago**

favorited **★ 3**
times

Post



This work is licensed
 under a **Creative
 Commons Attribution-
 ShareAlike 3.0
 Unported License.**

```
}  
delay(100);  
}
```